

## 1 Objective :-

To familiarize with measuring and testing equipments like multimeter, CRO, Function generator, Power supply, etc and also familiarize with bread board, resistors and capacitors, etc. Calculate the resistance value a/c to colour band & then verify with multimeter.

## 2 Observation Table :-

S.No	Resistor	Colour Band	Calculated value (in $k\Omega$ )	Measured value (in $k\Omega$ )
1	$R_1$	Green		
		Red	$= 82 \times 10^2 \pm 5\%$	$= 8.09 k\Omega$
		Red	$= 8.2 k\Omega$	
		Gold		
2	$R_2$	Yellow		
		Violet	$= 47 \times 10^3 \pm 5\%$	
		Orange	$= 47 k\Omega$	$= 46 k\Omega$
		Gold		
3	$R_3$	White		
		Red	$= 92 \times 10^1 \pm 5\%$	$= 0.8 k\Omega$
		Blue	$\approx 0.92 k\Omega$	
		Gold		
4	$R_4$	Red		
		Red	$= 22 \times 10^3 \pm 5\%$	
		Orange	$= 22 k\Omega$	$= 21.6 k\Omega$
		Gold		

- 1) Aim :- To verify the kirchhoff's current law (KCL).
- 2) Objective :- The objective of this lab activity is to verify kirchhoff's current law using mesh and nodal analysis.
- 3) Theory :- According to KCL, in any network of wires carrying currents, the algebraic sum of all current meeting at a junction is zero.

S.NO	Equipment	Specification	Quantity
1	Regular power DC supply	0 - 24V	1
2	PMMC Ammeter	0 - 1 A	3
3	Resistances / Rheostats		4
4	Connecting wires		


- 4) Procedure :- Four resistance  $R_1, R_2, R_3$  and  $R_4$  & ammeter  $A_1, A_2$  and  $A_3$  are connected to DC battery or regulated DC power supply as shown in figure.
- 5) Working principle :- The algebraic sum of current in a network of conductors meeting at a point is zero. This principle can be stated that:—  $\sum_{k=1}^N I_k = 0$
- 6) Key Parameters :- Let  $R_1 = 220\Omega, R_2 = 1k\Omega, R_3 = 330\Omega, R_4 = 330\Omega$  and also calculate:—  $\text{error} = \frac{\text{Actual} - \text{Measured}}{\text{Actual}} \times 100$

- 7) Experimental Results :-
- a) Calculate the ideal voltages and current for each element in the circuit & compare them to the measured value.
- b) Compute the percentage error in the two measurements.

#### 8) Precautions:-

- All connections should be tight.
- Reading & calculation should be taken carefully.
- Don't touch the live terminals.

→ Circuit Diagram :-

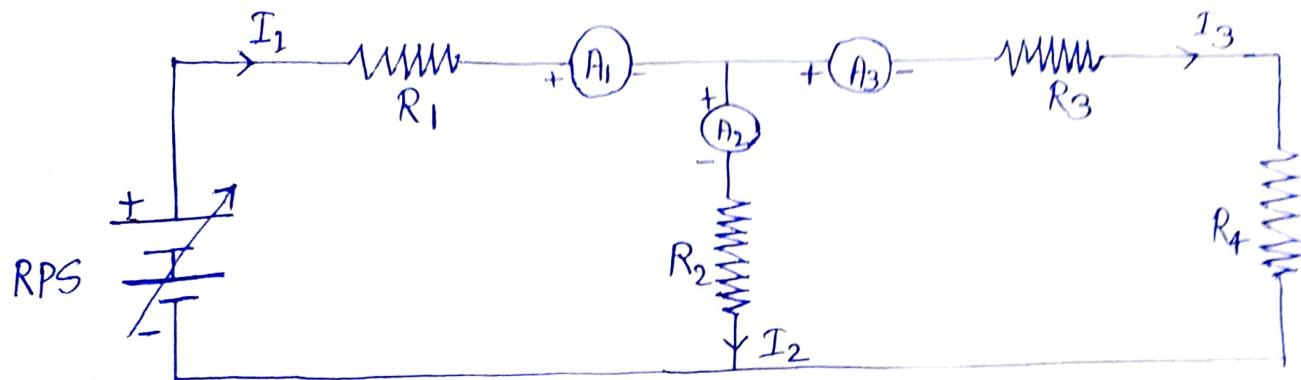

5) Observations :-

S.No	Reading of Ammeter $A_1$ ( $I_1$ )	Reading of Ammeter $A_2$ ( $I_2$ )	Reading of Ammeter $A_3$ ( $I_3$ )	$I_2 + I_3$
1	0.747	0.271	0.474	0.74
2	1.98	0.344	0.696	1.095

- 1) Aim :- To verify the kirchhoff's voltage law (KVL).
- 2) Objective :- The objective of this lab to verify KVL using mesh and nodal analysis of the given circuit.
- 3) Theory :- A/c to KVL, in any closed circuit or mesh, the algebraic sum of emf acting in the circuit or mesh is equal to the algebraic sum of the products of currents & resistance of each part of the circuit or mesh.

4) Apparatus Required :-


S.No	Equipment	Specification	Quantity
1	Regulated power DC supply	0 - 24 V	1
2	PMMC Voltmeters	0 - 24 V	4
3	Resistances		4
4	Connecting wires		

6) Procedure :- Resistances  $R_1, R_2, R_3$  &  $R_4$  & Voltmeters  $V_1, V_2, V_3$  &  $V_4$  are connected to DC battery as shown in figure. Three rheostat are set their maximum values, supply is switched on and the reading of the voltmeters  $V_1, V_2, V_3$  &  $V_4$  is noted. The process may be repeated by varying either of resistances  $R_1, R_2, R_3$  &  $R_4$ .

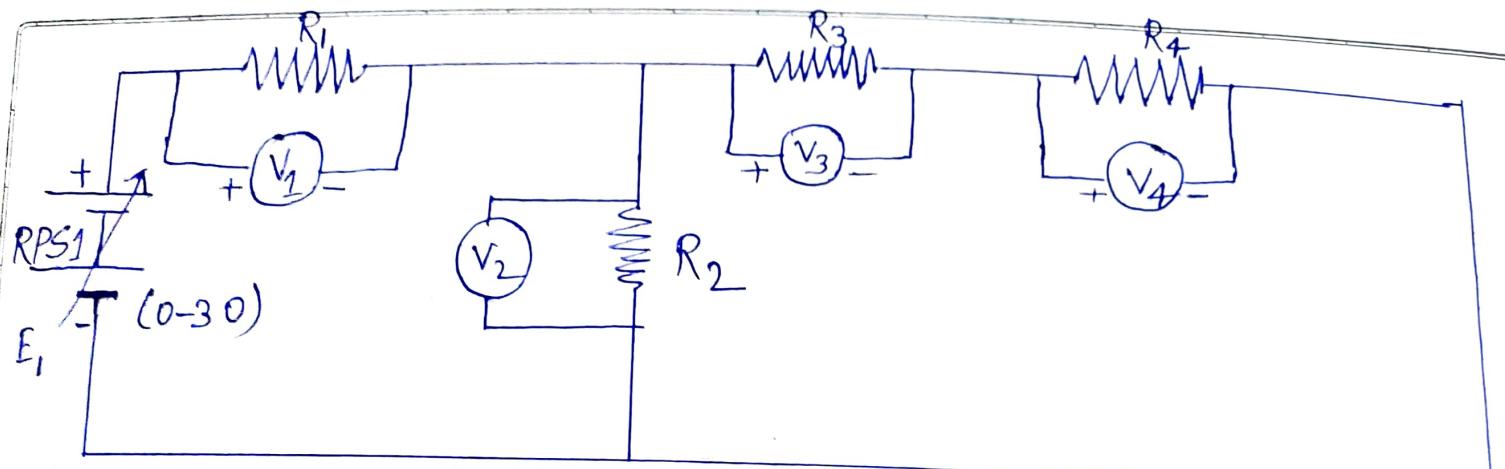7) Working principle :- The sum of the emfs in any closed loop is equivalent to the sum of the potential drop in that loop. Similar to KCL, it can be stated as :-

$$\sum_{k=1}^N v_k = 0$$

\* Key parameters :- Let  $R_1 = 220\Omega, R_2 = 1k\Omega, R_3 = 330\Omega, R_4 = 330\Omega$  and also calculate the error =  $\frac{\text{Actual} - \text{Measured}}{\text{Actual}} \times 100$



KVL Circuit Diagram

S.No	Reading of Voltmeter $V_1$	Reading of Voltmeter $V_2$	Reading of Voltmeter $V_3$	Reading of Voltmeter $V_4$	$V = V_1 + V_2$	$V_2 = V_3 + V_4$
1	7.42	2.74	0.47	2.213	10.14	2.74
2	10.44	4	0.69	3.31	14.44	4

## 8) Experiment Result :-

- Calculate the ideal voltages and currents for each element in the circuit and compare them to the measured values.
- Compute the percentage error in the two measurements and provide a brief explanation for the error.

## 9) Precautions :-

- All connections should be tight.
- All steps should be followed carefully.
- Reading and calculations should be taken carefully.
- Don't touch the live terminals.

1) Aim :- To verify the Norton's Theorem.

2) Apparatus Required :-

S.No	Equipment	Specification	Quantity
1	Two regulated DC power supply	0-12 V 10-5A	1
2	PMMC Voltmeter	0-10 V	1
3	PMMC Ammeter	0-5 A	1
4	Resistances/Rheostats		4/1
5	Connecting wires		

3) Brief Theory :- According to this theory if a resistor of  $R_L$  ohms be connected between any two terminals of a linear bilateral network, then the resulting current through load resistor will be equal to  $\frac{R_{TH}I_{SC}}{R_L + R_{TH}}$  where  $I_{SC}$  is the short circuit current through load  $R_L + R_{TH}$  terminal points &  $R_N = R_{TH}$  is the resistance of network measured between these two points.


4) Procedure :-

- Remove the resistance
- Find the short circuit current  $I_{SC}$  which flows through two load terminals from where resistance is removed
- Compute the resistance of whole network as looked into from these two terminals after all sources of emf are treated as shorted.
- Finally, calculate the current flowing through  $R_L = I_L = \frac{R_{TH}I_{SC}}{R_L + R_{TH}}$


5) Observation :-

S.No	Short circuited current through load terminal $I_{SC}$	Req across the Load terminals, $R_{TH}$	$I_L = \frac{R_{TH}I_{SC}}{R_L + R_{TH}}$	% error Measured $I_L$
1	0.42	0.48	0.401	2.69
2	0.59	0.63	0.59	3.38


#Circuit Diagram :-

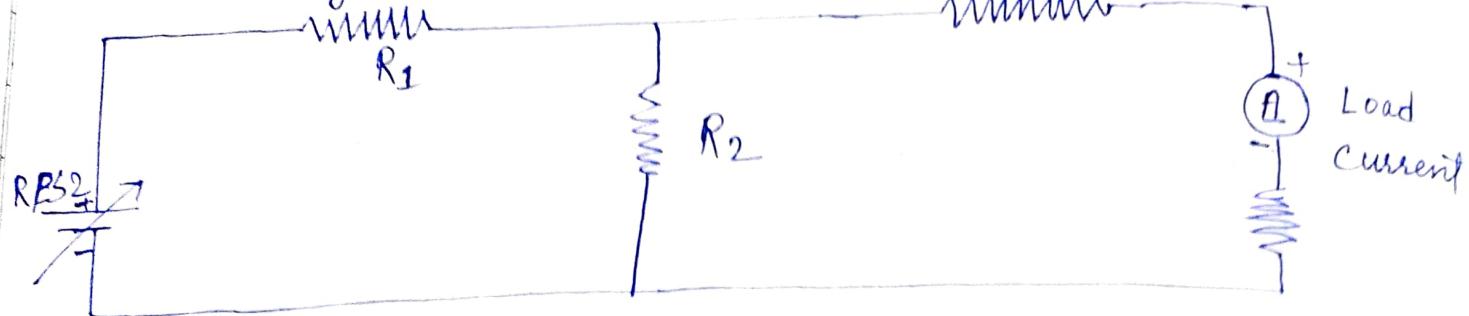


#To find  $V_{TH} = V_{TH}$

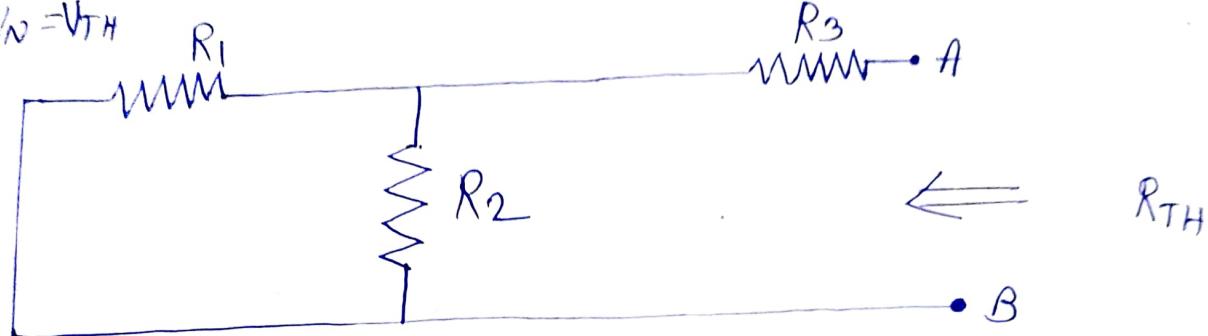

#To find  $I_{SC}$

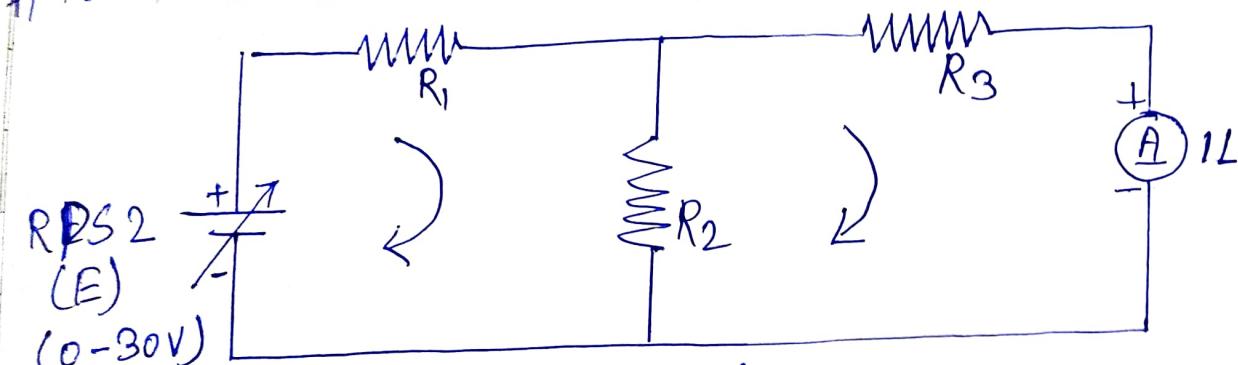

#Norton's Equivalent circuit :-

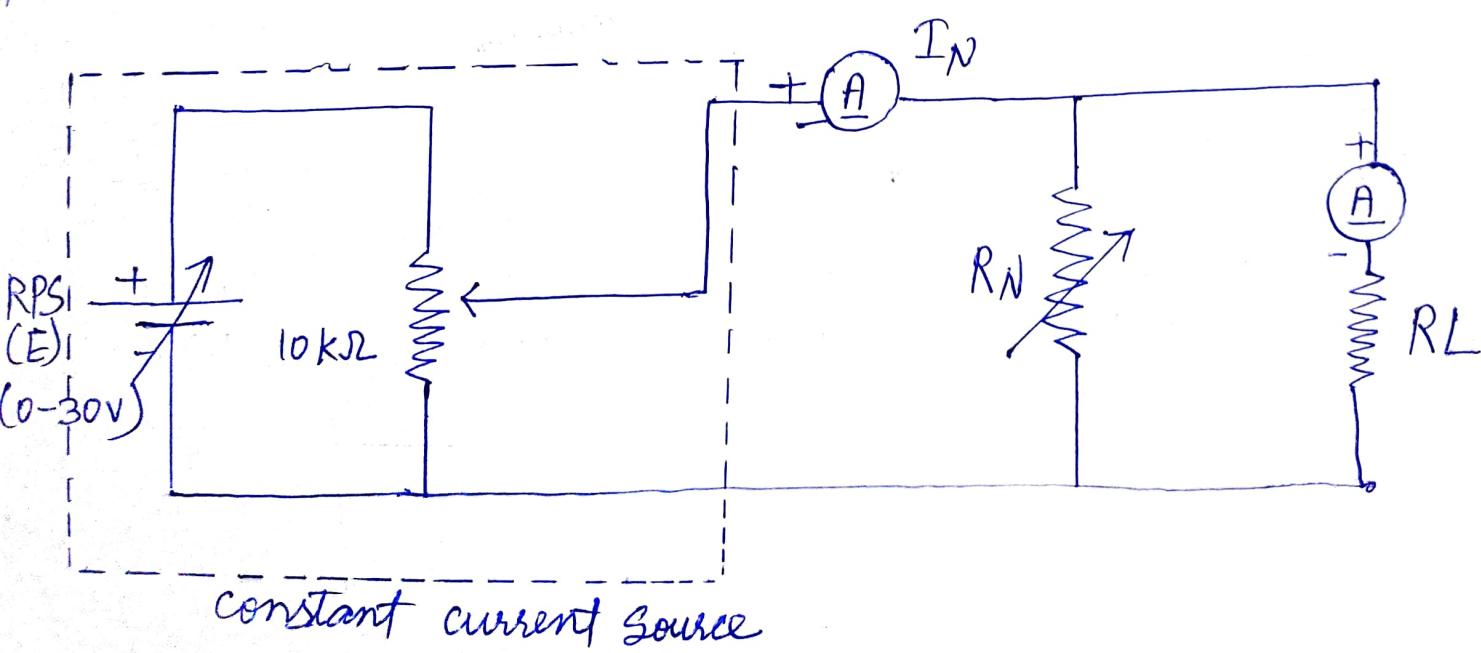

## 7) Result and Discussion:-

- i) The value of short circuit current  $I_{sc}$  is 1..... Amp.
- ii) The value of Norton's resistance is \_\_\_\_\_ ohms.
- iii) It will be found that measured value of current flowing through the load  $I_L$  is the same as determined by Norton's theorem.

## 8) Outcomes:-

Students are able to analyze Norton's theorem in resistive circuit.

## 9) Precautions:-

All connection should be tight.

All steps should be followed properly.

Reading & calculation should be taken carefully.

Don't touch the live terminals.

1) Aim:- To verify the Thevenin's Theorem.

2) Apparatus Required:-

S. No Equipment

1 Two Regulated DC power supply

2 PMMC Voltmeter

3 PMMC Ammeter

4 Resistances / Rheostats

5 Connecting wire

Specification	Quantity
0-12V 10-6V	1
0-12V 10-6V	1
0-10V	1
0-5A	1
	4/1

3) Brief theory:- A/c to this theorem if a resistor of  $R_L$  ohms be connected b/w any two terminals of a linear bilateral network, then the resulting current through the load resistor will be equal to  $\frac{V_{TH}}{R_L + R_{TH}}$  where  $V_{TH}$  is the P.d across these two points &  $R_{TH}$  is the resistance of network measured b/w two points.  $V_{TH}$  is the open circuit voltage across the terminals,  $R_{TH}$  is the equivalent resistance across the terminals,  $R_L$  is the load resistance.


5) Procedure:-

- Remove the resistance (called Load Resistance  $R_L$ ).
- Find the open circuit voltage  $V_{OC}$  which appears across the two terminals from where resistance is removed. It is called Thevenin's voltage
- Finally, calculate the current flowing through  $R_L$  using eqn =  $\frac{V_{TH}}{R_L + R_{TH}}$


6) Observation:-

S. No	Open circuit voltage across Req across the load Load $R_L$ terminals ( $V_{OC}$ )	Req across the load $R_L$ terminals $R_{TH}$	Load current $I_L = \frac{V_{TH}}{R_L + R_{TH}}$	Measured $I_L$
1	9.2	130.5	15.8	15.8


# Circuit Diagram:-  $R_1$

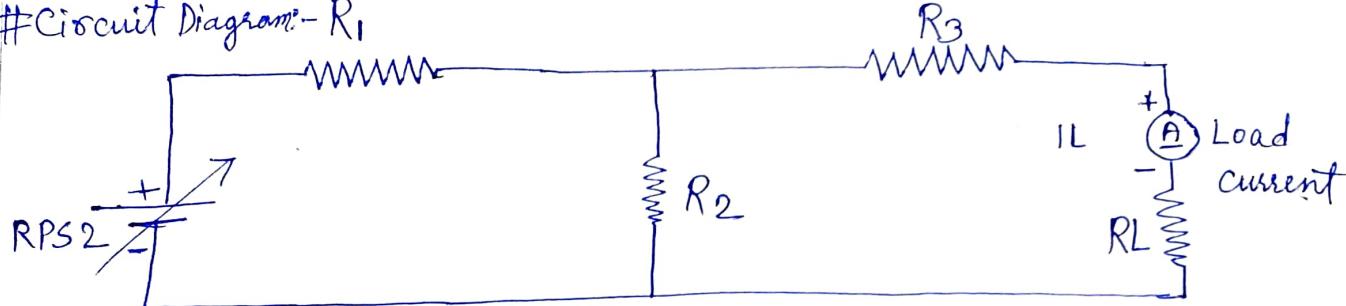


# To find  $V_m$

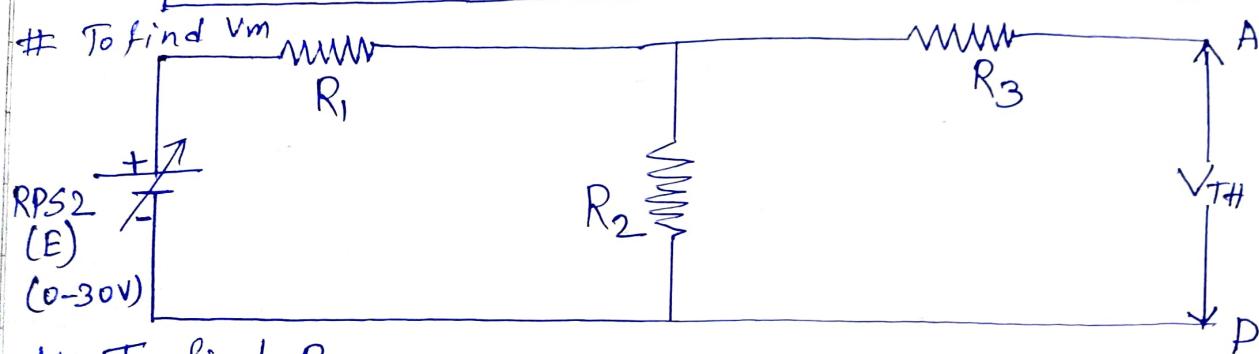

# To find  $R_{TH}$

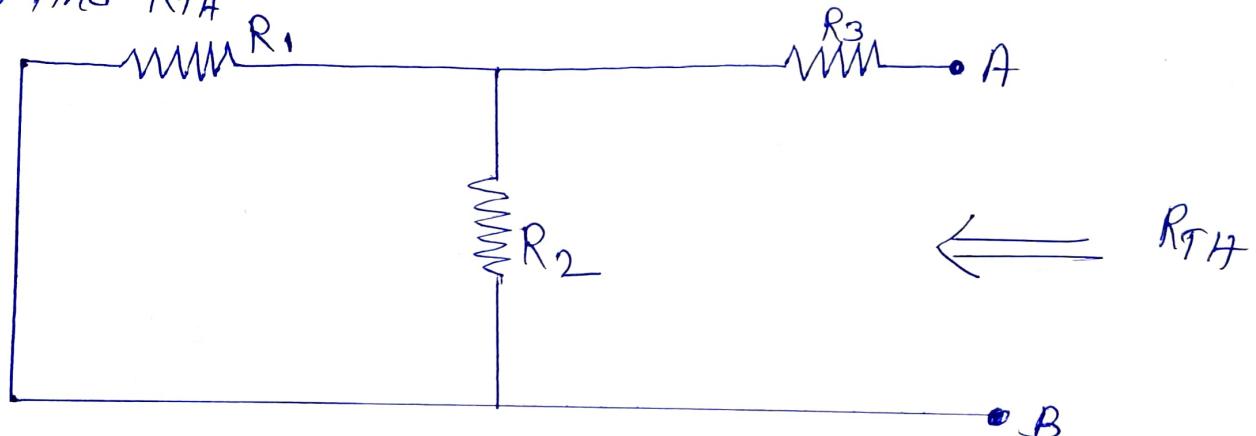

# Thevenin's Equivalent circuit:-

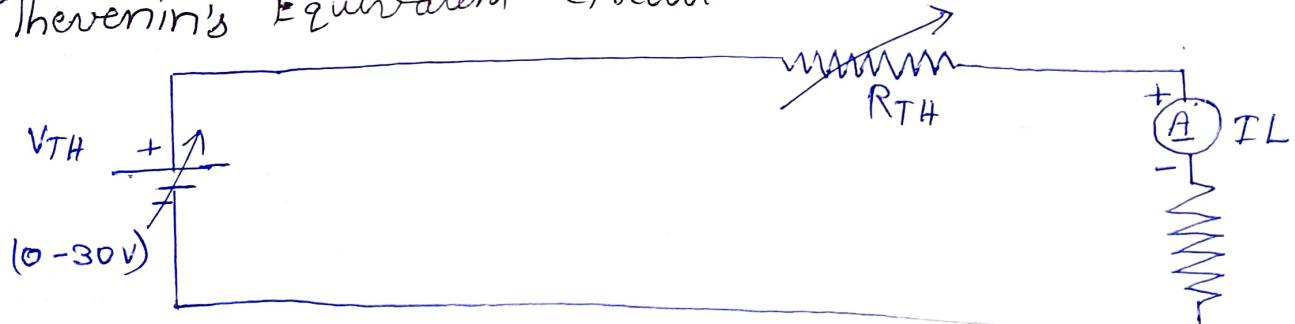

## 7) Result and Discussion:-

- a) The value of open circuit voltage ( $V_{OC}$ ) is \_\_\_\_\_ volts.
- b) The value of Thevenin's resistance is \_\_\_\_\_ ohms.
- c) The value of current across load is \_\_\_\_\_ amps.
- d) It will found that measured value of current flowing through the load  $I_L$  is the same as determined by Thevenin's Theorem.

## 8) Outcomes :-

Students are able to analyze Thevenin theorem in presence of DC source.

## 9) Precautions :-

- a) All connection should be tight.
- b) All steps should be followed carefully.
- c) Reading and calculations should be taken carefully.
- d) Don't touch the live terminals.